



V, I, R measurements: how to generate and measure quantities and then how to get data (resistivity, magnetoresistance, Hall).

590B

Makariy A. Tanatar

November 10, 2008

SI units/History

Resistivity

Typical resistivity temperature dependence



First reliable source of electricity
Alternating plates of Zn and Cu separated by cardboard soaked in saltwater


Electrical action is proportional to the number of plates



Alessandro Giuseppe Antonio Anastasio Volta
1745-1827
Count (made by Napoleon 1810)
1881- Volt unit adopted internationally




André-Marie Ampère
1775 - 1836

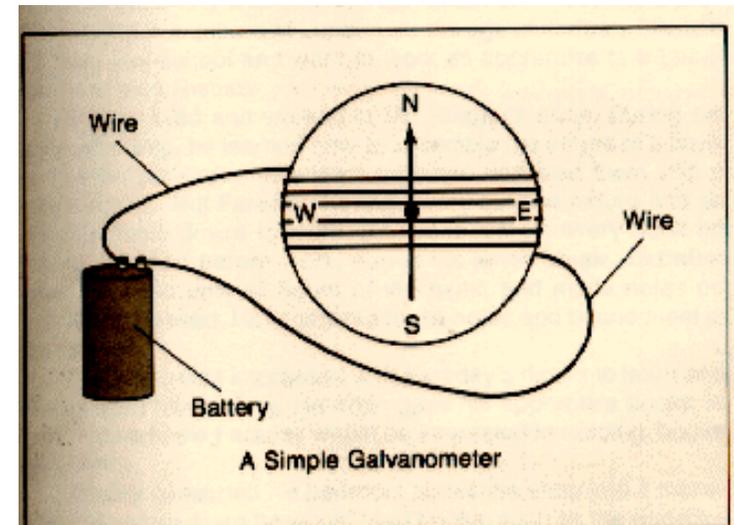


Months after 1819 Hans Christian Ørsted's discovery of magnetic action of electrical current

1820 Law of electromagnetism (Ampère's law)
magnetic force between two electric currents.

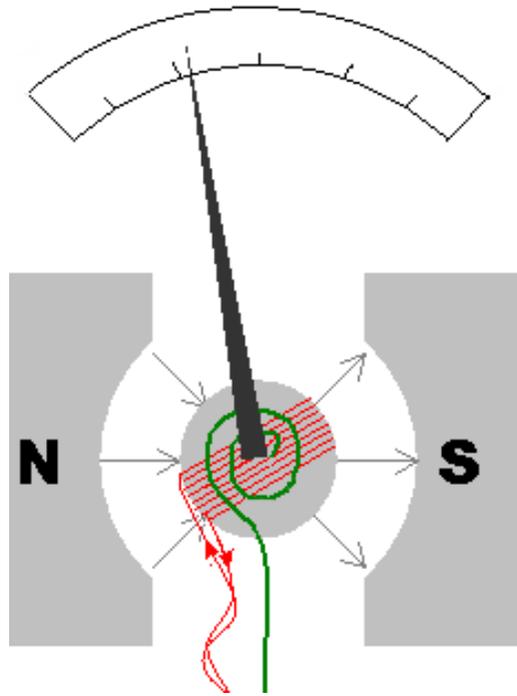First measurement technique for electricity
Needle galvanometer



D'Arsonval galvanometer

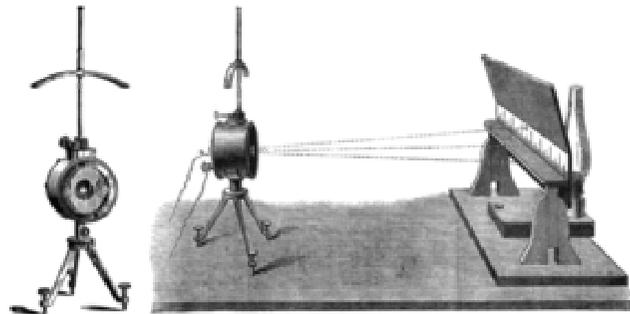

Thompson (Kelvin) mirror galvanometer

Can be measured via
Magnetic action of electric current
Heat
Mass flow (electrolysis)
Light generation
Physiological action (Galvani,
You can do anything with cats!)



Ampere main SI unit:

Definition based on force of
interaction between parallel current

Replaced recently

Amount of deposited mass per
unit time in electrolysis process




Georg Simon Ohm
1789 - 1854

$$I = V/R$$

1826 Ohm's apparatus

Current measurement:
magnetic needle

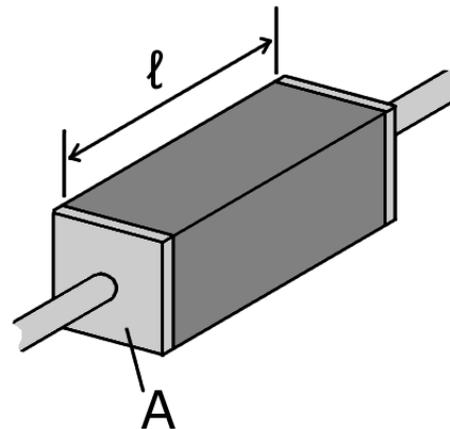Voltage source:
thermocouple (Seebeck 1821)
Steam heater
Ice cooler



Resistivity


$$\rho = R \frac{A}{\ell}$$




Our common experience: resistance is the simplest quantity to measure

True, but only inside "comfort zone"


Use Ohm's law

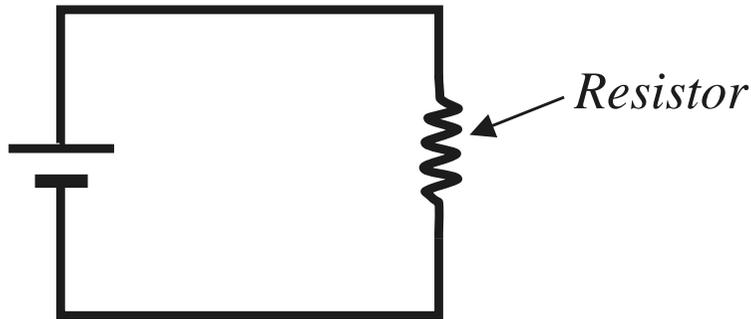

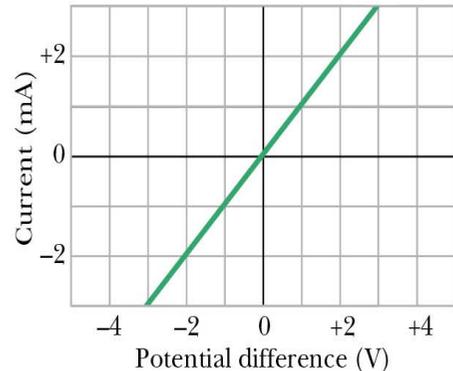Apply known I (V) Measure V (I)
Calculate resistance



(b)

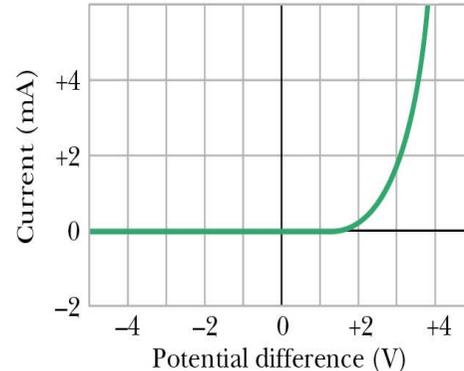

(c)

Implicit: Ohm's law is valid for our measurement object, I-V curve is linear

May be far from true!

Implicit: our whole circuit is linear and no offsets!

Assumption: wire resistance is negligible

Digital Multi Meters -DMM




Typical characteristics
1 mV per last digit
1 μ A per last digit
High input offset current
Low input impedance



Resistance 4-probe measurements (Kelvin probe measurement)


To minimize wire resistance effect for remote objects
To minimize the effect of contacts for resistivity measurements
Even allows slightly rectifying contacts
And "high" resistance contacts

FIGURE 3-15: Four-Wire Resistance Measurement

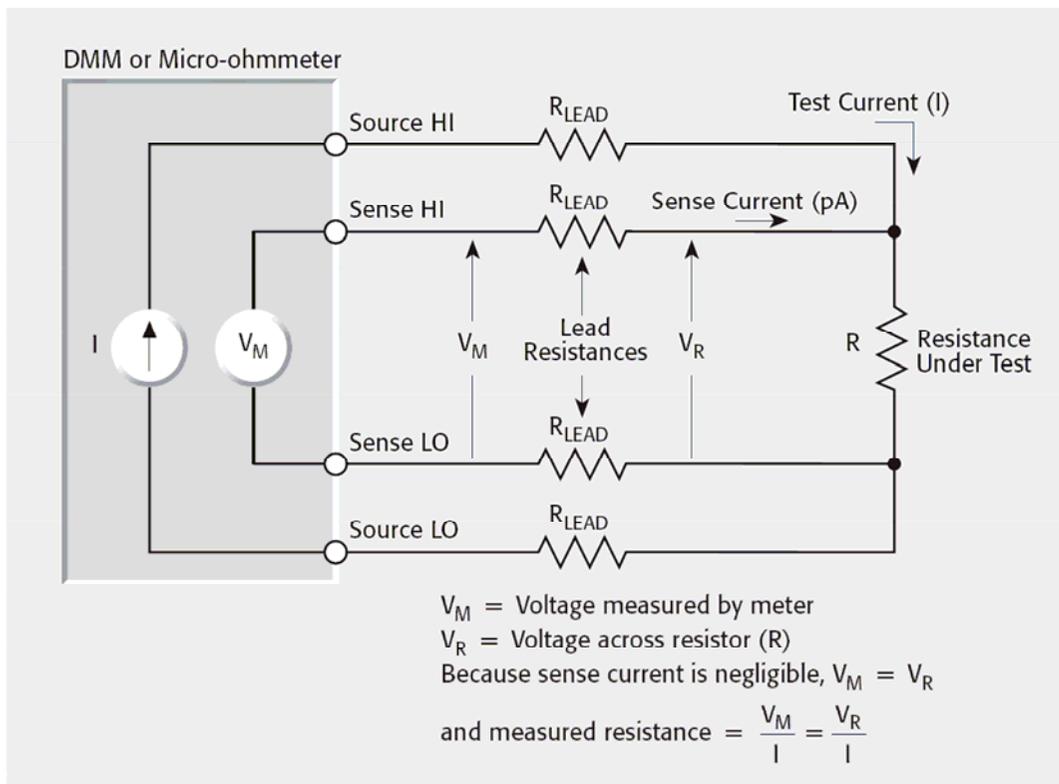

Current source in one circuit
Potential voltage measurement
in ANOTHER circuit

FIGURE 2-31: Constant-Current Method Using a Separate Current Source and Voltmeter

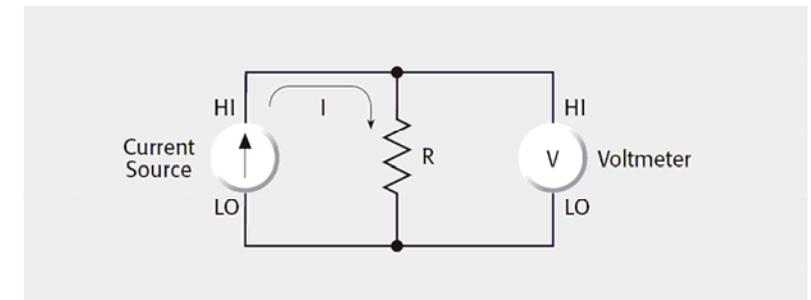


Thanks Adam!



Resistance: bridge measurement

At balance $I = 0$


$$Z1 \cdot Z4 = Z2 \cdot Z3$$

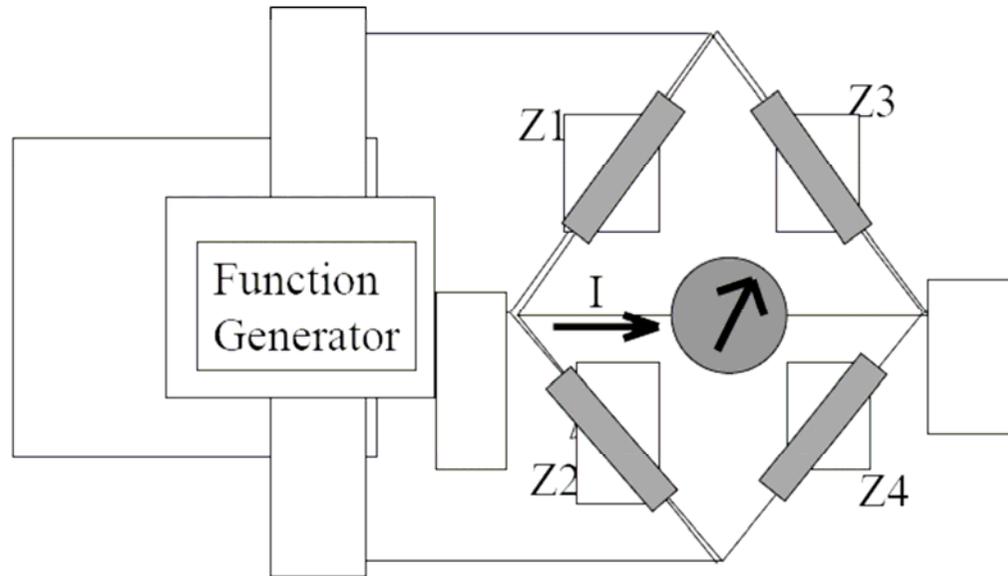

Replaces I and V measurement by resistance compensation to obtain zero reading
No effect of circuit non-linearity,
In old days PRECISE DIGITAL measurement

Does not go well with modern electronics

Slide Wire Wheatstone Bridge

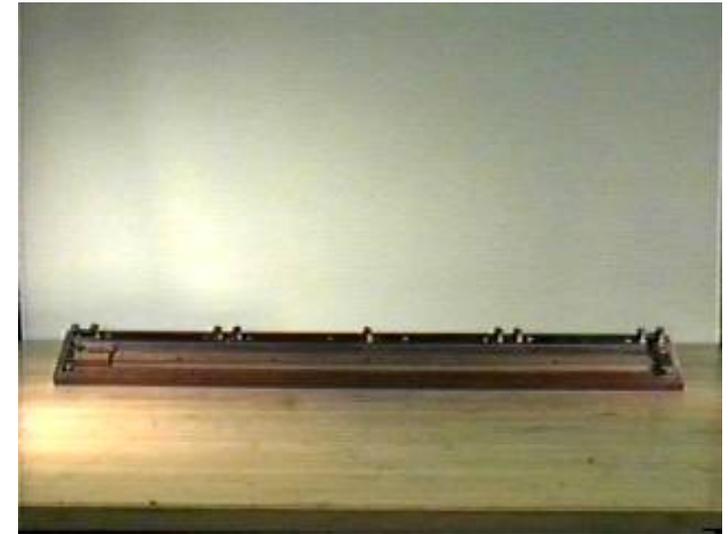

Resistance Decade Bridge





FIGURE 1-2: Theoretical Limits of Voltage Measurements


Johnston noise

voltage

$$E = \sqrt{4kTRB} \text{ volts, rms}$$

current
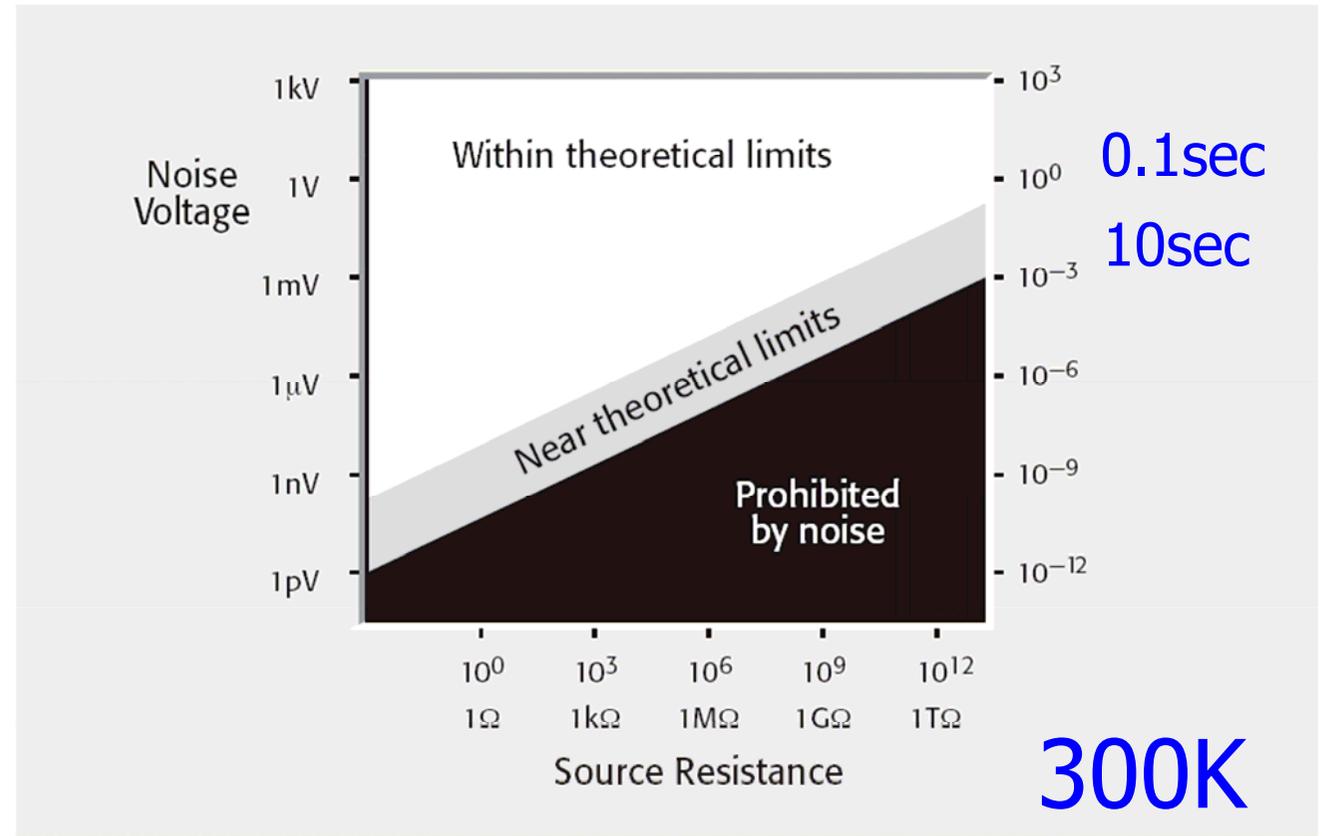
$$I = \frac{\sqrt{4kTRB}}{R} \text{ amperes, rms}$$





Going outside comfort zone: DC measurements

Special designs

High impedance source Electrometer

Used for $I < 10 \text{ nA}$, $G > 1 \text{ G}\Omega$

Input impedance $\sim 100 \text{ T}\Omega$


Input offset current $< 3 \text{ fA}$

Capable of R measurement up to $300 \text{ G}\Omega$

Low impedance source- Nanovoltmeter
 $< 1 \text{ nV}$

Source-measure units for
resistance measurements

FIGURE 1-3: Typical Digital Multimeter (DMM), Nanovoltmeter (nVM), Nanovolt Preamplifier (nV PreAmp), and Electrometer Limits of Measurement at Various Source Resistances

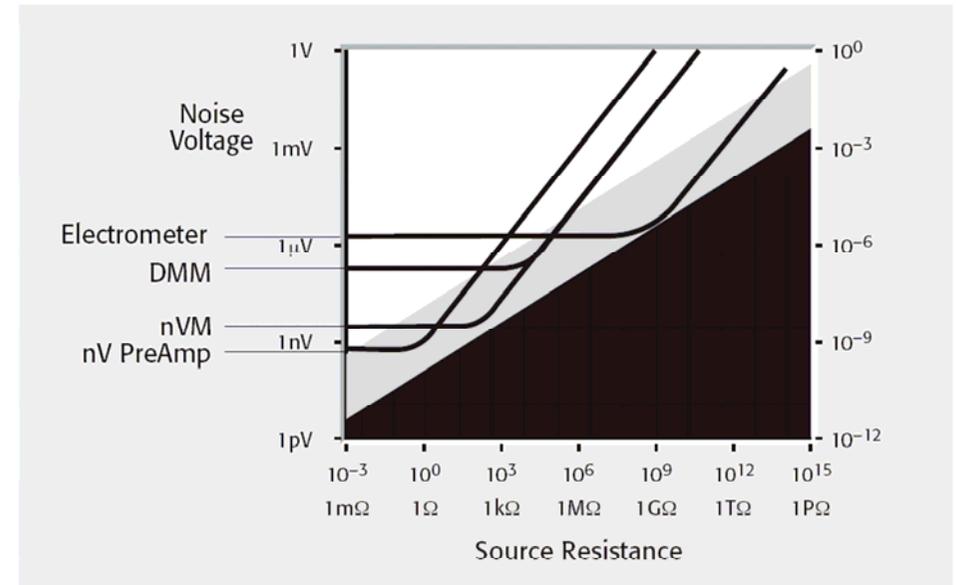

Here DMM
is from Keithley,
not from Fluke!

www.keithley.com

LLM

6th
Edition

Low Level Measurements Handbook

Precision DC Current, Voltage, and Resistance Measurements



High resistance measurements

Special features: Guarded cables
Triaxial connectors

FIGURE 2-34a: Effects of Cable Resistance on High Resistance Measurements

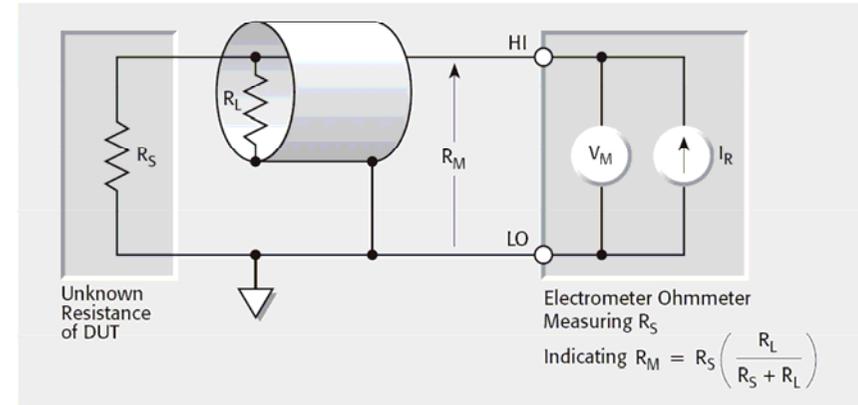


FIGURE 2-34b: Equivalent Circuit of Figure 2-34a Showing Loading Effect of Cable Leakage Resistance R_L .


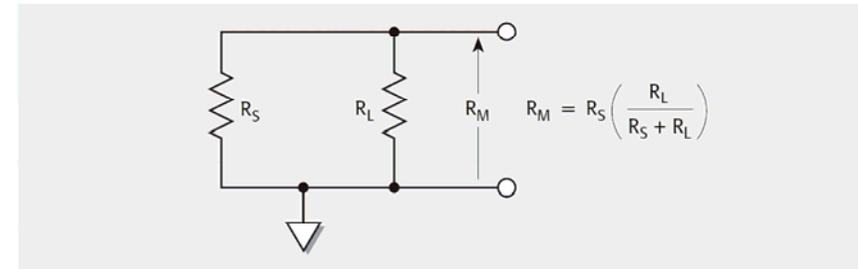


FIGURE 2-34c: Guarding Cable Shield to Eliminate Leakage Resistance

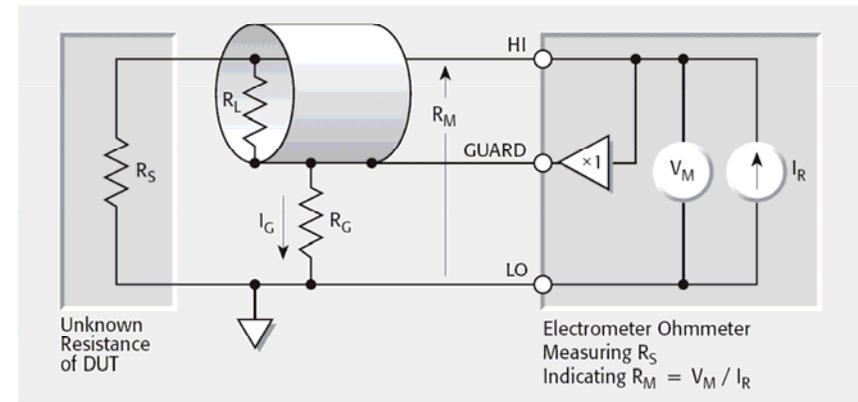

www.keithley.com

LLM

6th
Edition

Low Level Measurements Handbook

Precision DC Current, Voltage, and Resistance Measurements



High resistance measurements

Because of parasitic capacitance and high impedance only DC measurements

Important to make correct electrometer connections

FIGURE 2-40: Proper Connection

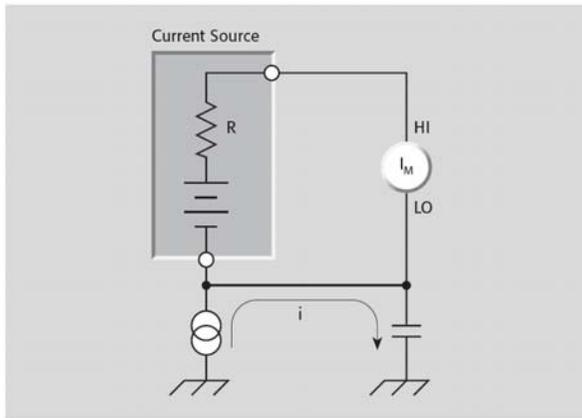


FIGURE 2-41: Improper Connection

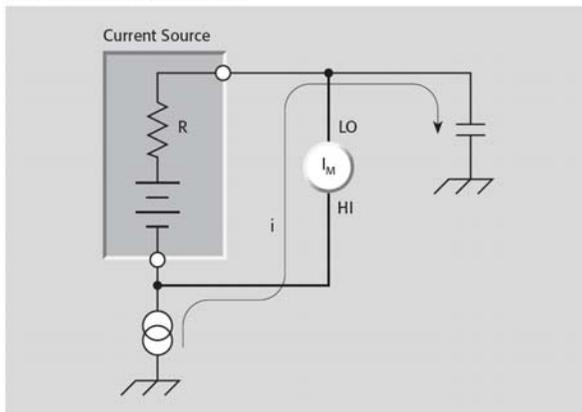


FIGURE 2-35: Settling Time is the Result of $R_S C_{SHUNT}$ Time Constant


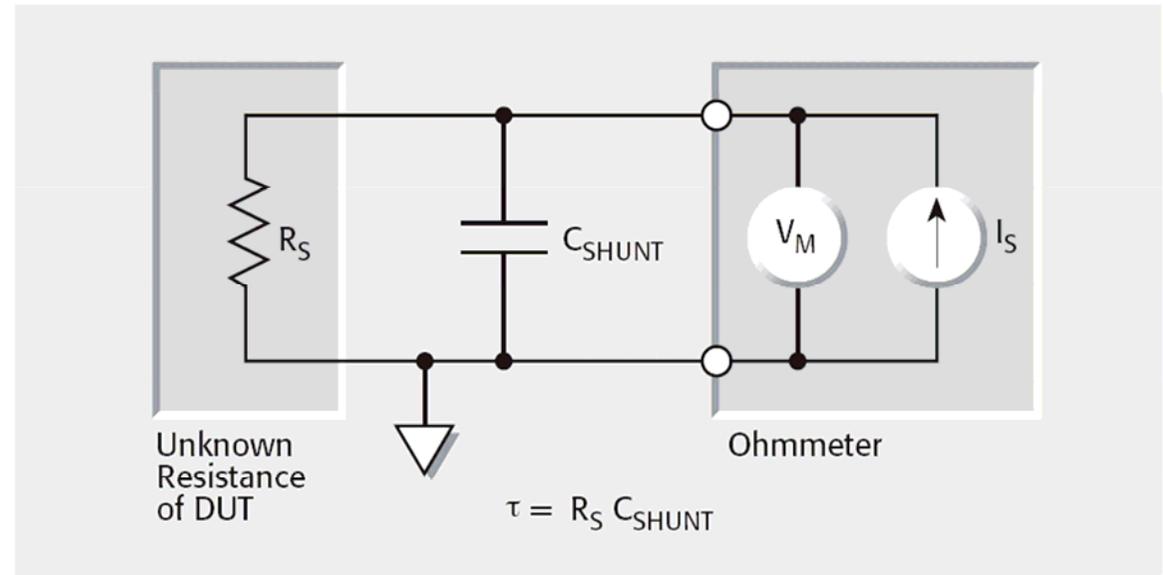


FIGURE 2-36: Exponential Settling Time Caused by Time Constant of Shunt Capacitance and Source Resistance

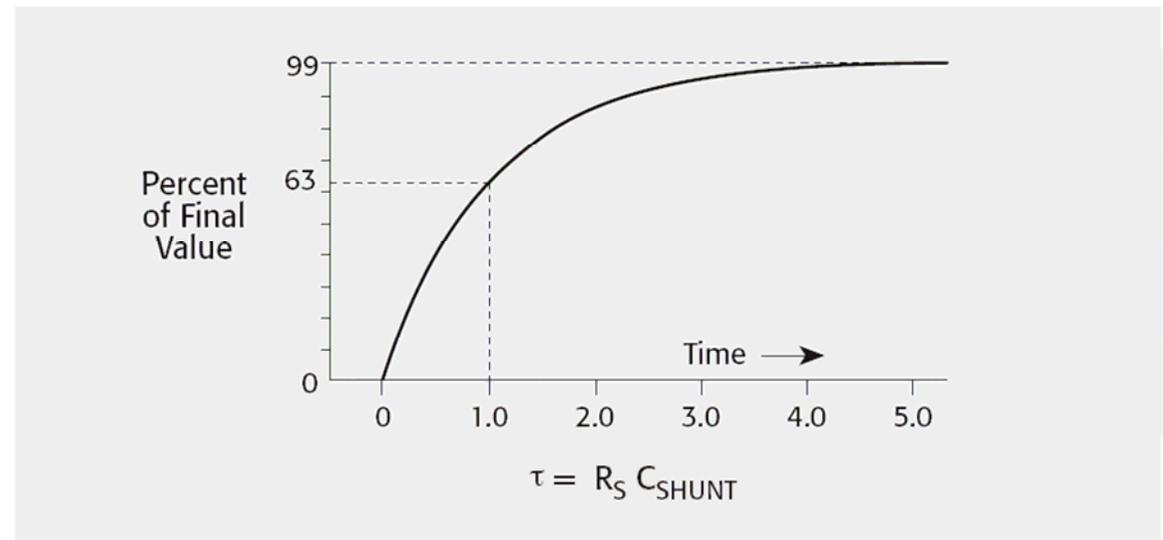




High resistance measurements


Guard ring technique:

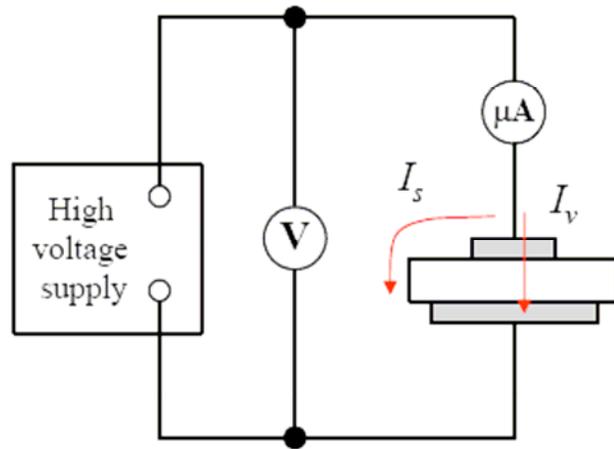- Volume resistance, R_V
- Surface leakage resistance, R_S



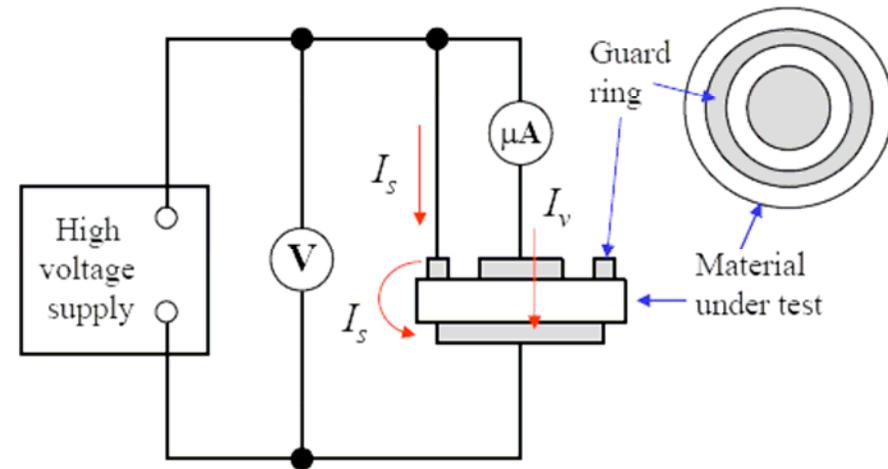(a) Circuit that measures insulation volume resistance in parallel with surface leakage resistance

$$R_{meas} = R_s // R_v = \frac{V}{I_s + I_v}$$



(b) Use of guard ring to measure only volume resistance

$$R_{meas} = R_v = \frac{V}{I_v}$$



Low resistances

Sources of errors:

- Offset voltages of electronics
- Thermoelectric EMFs
Important in cryogenic measurements
Avoid dissimilar materials in design
In Dilution Fridges frequently find different pairs of wires, superconducting and high resistance. Never mix!!!
- Magnetic field interference
Twisted pairs,
Mechanical stability

FIGURE 3-4: Reversing Sources to Cancel Thermoelectric EMFs


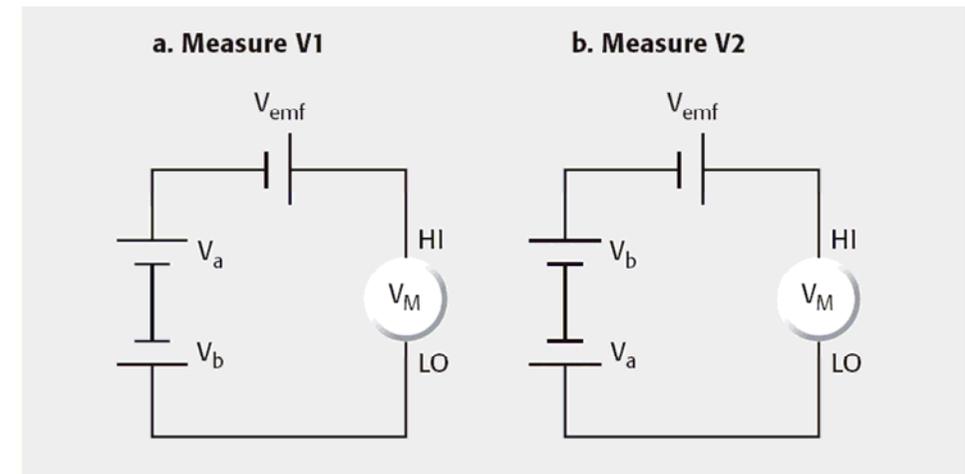


FIGURE 3-10: Minimizing Interference from Magnetic Fields

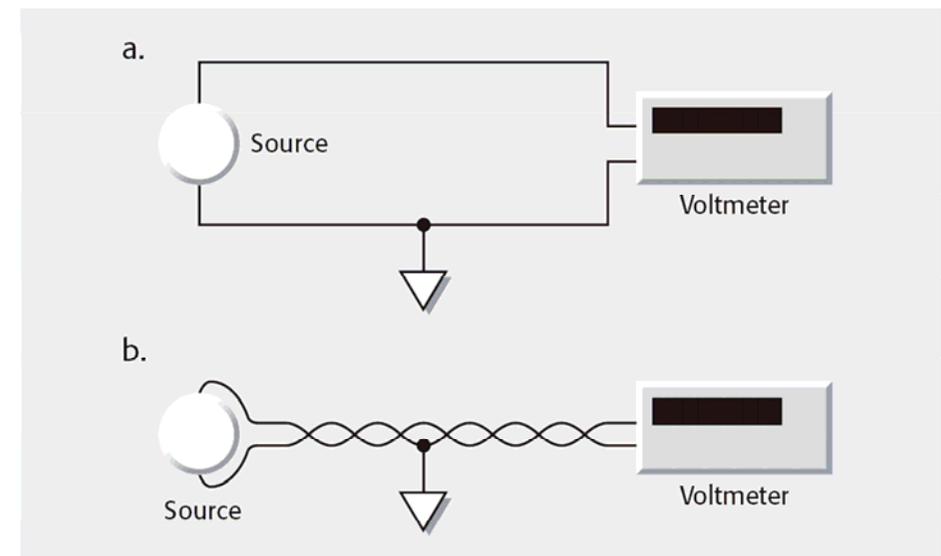

www.keithley.com

LLM

6th
Edition

Low Level Measurements Handbook

Precision DC Current, Voltage, and Resistance Measurements



Low resistances: AC may be a better choice

Lock-in resistance measurements
SR830
Built-in AC voltage generator


“Ohmic contacts” required for AC measurements

AC in differential mode
avoids offsets
Low frequency (below power grid, typically 10-20 Hz)

Problem: low input impedance,
Not good for high resistance sources

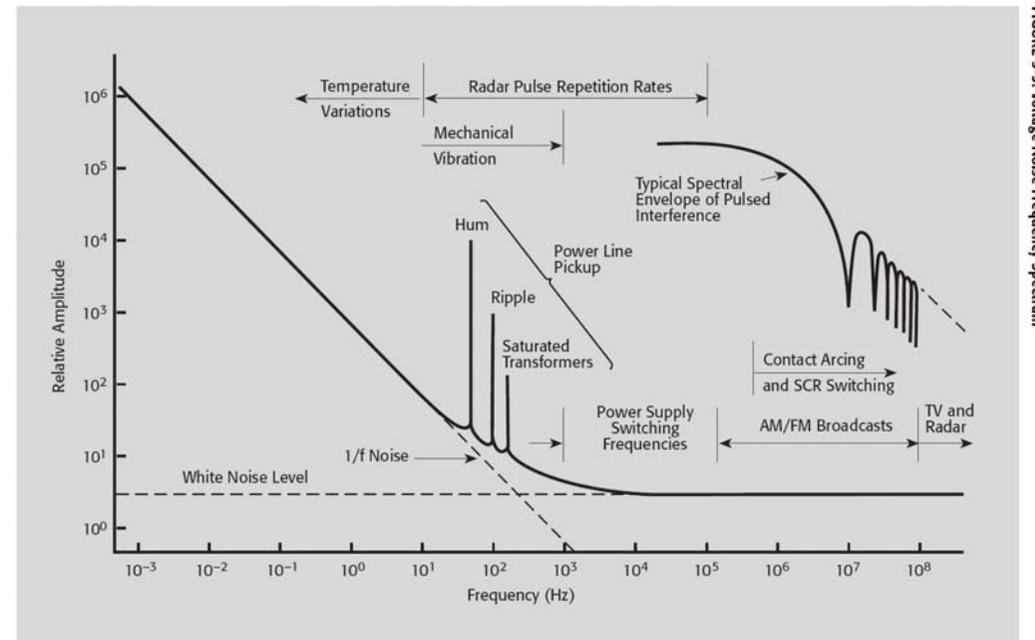Problem: current source is not precise

Very popular simple and reasonably
precise resistance measurement





Low resistances: AC may be a better choice

Resistance bridges

LR700, AVS47, SIM927 and LS370

Actually these are not bridges!

Do not use compensation

Ratiometric resistance measurement

Specialized for low-temperature
precision resistance measurements

- **Low noise**

- **Low excitation power**

- **AC**

Resistance measurements

AC to avoid offsets

Low frequency (below power grid, typically 10-20 Hz)

SIM927 Comparators measuring reference resistance voltage
and in-phase component of sample resistance voltage



Shielding, grounding

FIGURE 3-6: Shielding to Attenuate RFI/EMI Interference


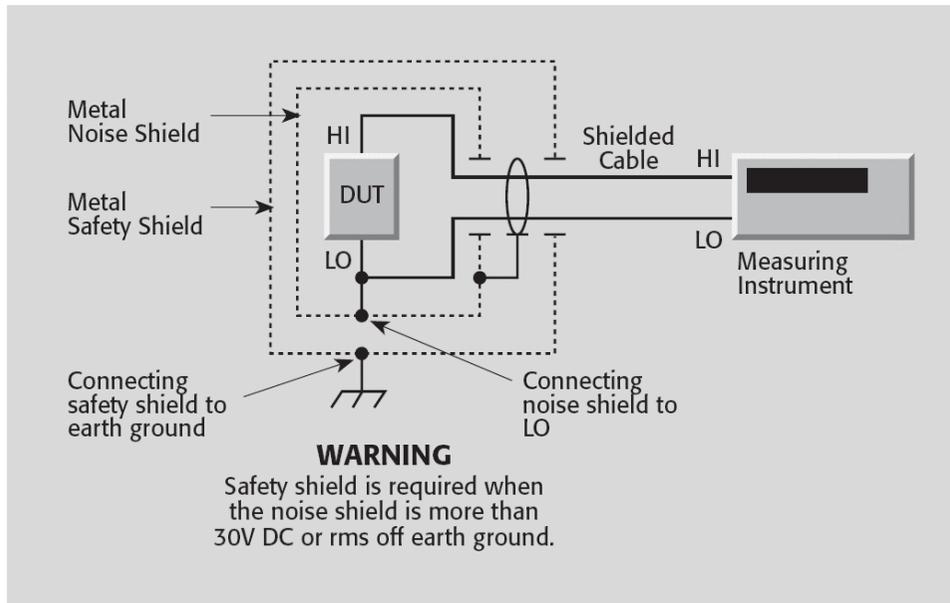


FIGURE 3-11a: Multiple Grounds (Ground Loops)

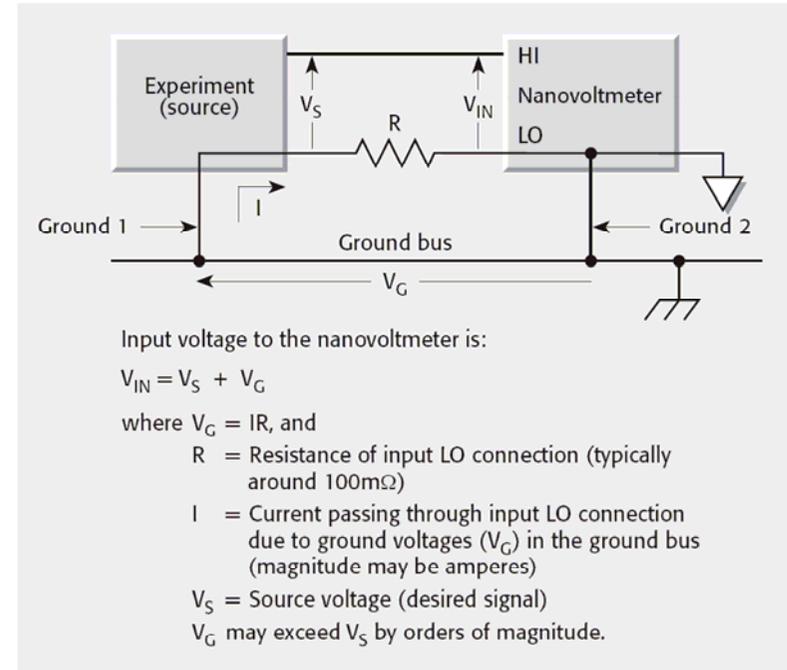

General rule

Avoid grounds in measurement circuits

Avoid common grounds with different devices



FIGURE 2-52: Noise Voltage vs. Bandwidth at Various Source Resistances

Ways to reduce noise:

Reduce bandwidth

- averaging (digital or analog)
- filtering

Very long term measurements are susceptible to other errors, Temperature drift

Cool down the source


300K to 3K

10 times noise decrease

Low temperature transformers and Preamplifiers in DR

Source resistance

Low resistance contacts

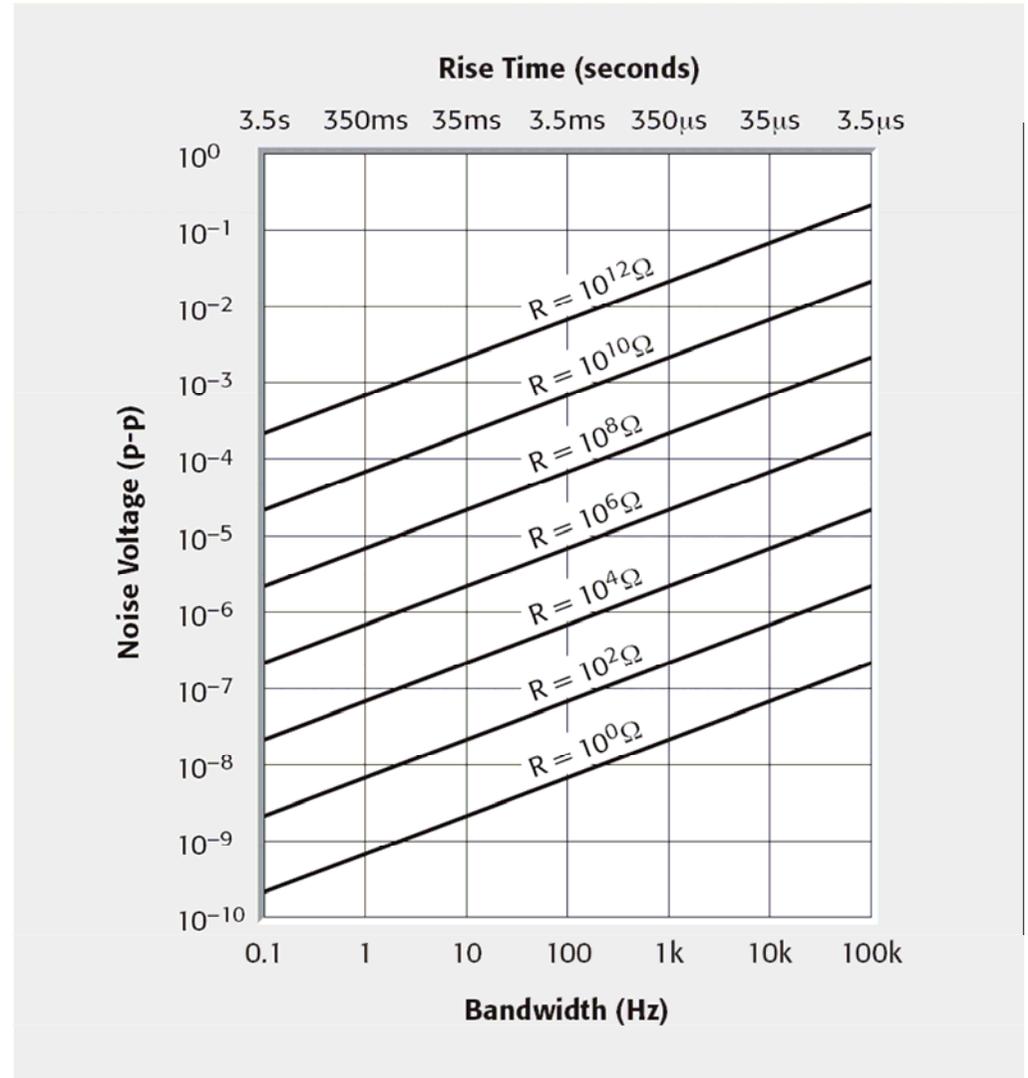



Resistivity measurements: 4-probe

“Ohmic contacts” required for AC measurements



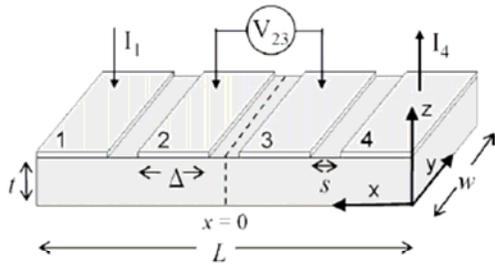



Figure 1. Schematic of the co-linear 4-probe configuration with electrodes that span the width of the specimen.

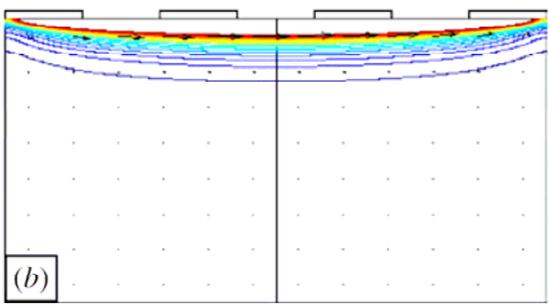

Strict requirements on sample shape

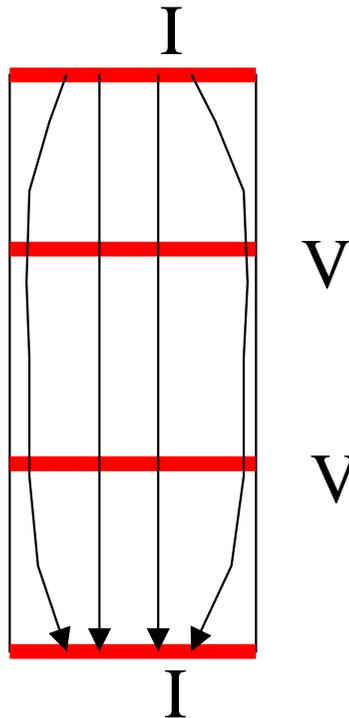

Probably most famous artefact

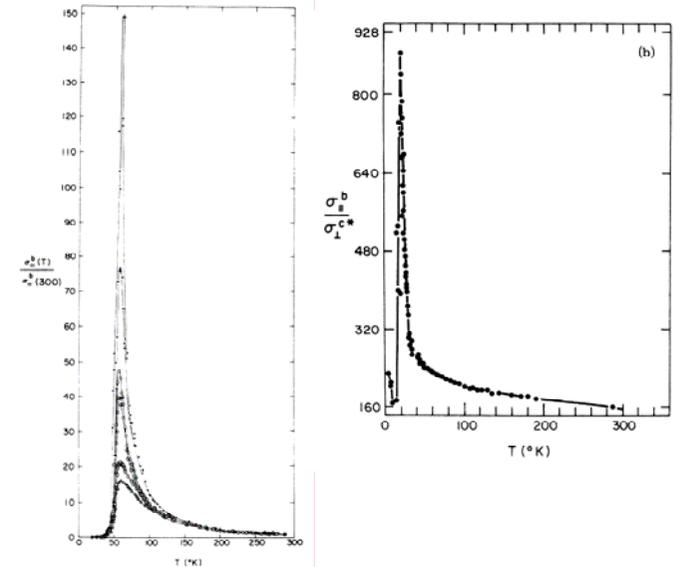

Concerns

Different I and V circuits

May be disconnected!


Potential contacts should be connected well to current path

Superconducting fluctuations and the peierls instability in an organic solid
SSC 12, 1125 (1973)




Four probe measurement in bridge configuration

Four-Terminal Resistor

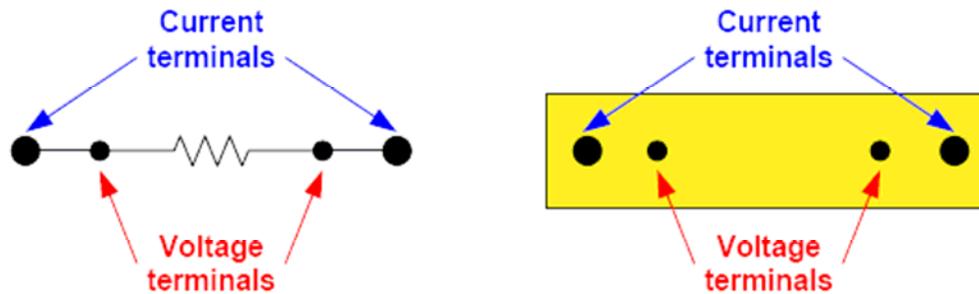

Four-terminal resistors have current terminals and potential terminals. The resistance is defined as that between the potential terminals, so that contact voltage drops at the current terminals do not introduce errors.

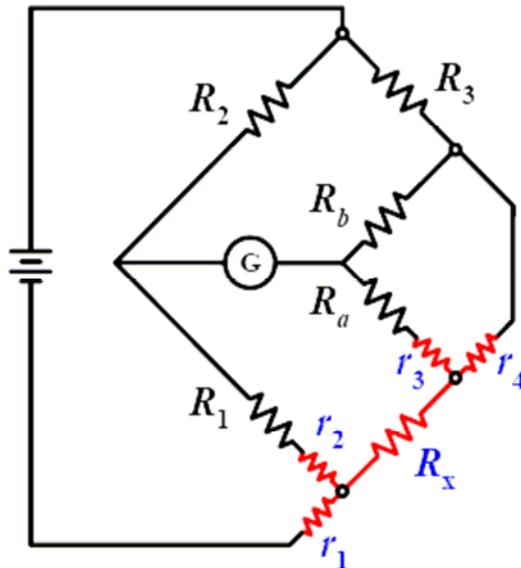Four-Terminal Resistor and Kelvin Double Bridge



- r_1 causes no effect on the balance condition.
- The effects of r_2 and r_3 could be minimized, if $R_1 \gg r_2$ and $R_a \gg r_3$.
- The main error comes from r_4 , even though this value is very small.



VOL. 13 No. 1

FEBRUARY 1958

Philips Research Reports

EDITED BY THE RESEARCH LABORATORY
OF N.V. PHILIPS' GLOEILAMPENFABRIEKEN, EINDHOVEN, NETHERLANDS

R 334

Philips Res. Repts 13, 1-9, 1958

A METHOD OF MEASURING SPECIFIC RESISTIVITY AND HALL EFFECT OF DISCS OF ARBITRARY SHAPE

by L. J. van der PAUW

537.723.1:53.081.7+538.632:083.9

Summary

A method of measuring specific resistivity and Hall effect of flat samples of arbitrary shape is presented. The method is based upon a theorem which holds for a flat sample of arbitrary shape if the contacts are sufficiently small and located at the circumference of the sample. Furthermore, the sample must be singly connected, i.e., it should not have isolated holes.



Resistivity measurements: van der Pauw method

Very popular in semiconductor industry
Does not require sample of regular shape

Assumptions


1. Homogeneous sample
2. Isotropic sample
3. Two-dimensional, thickness is unimportant
4. Sample boundary sharply defined

Surface resistance



$$\rho_{\square} = \frac{\pi}{\ln 2} \frac{R_{ab-cd} + R_{bc-da}}{2} f$$

Resistivity
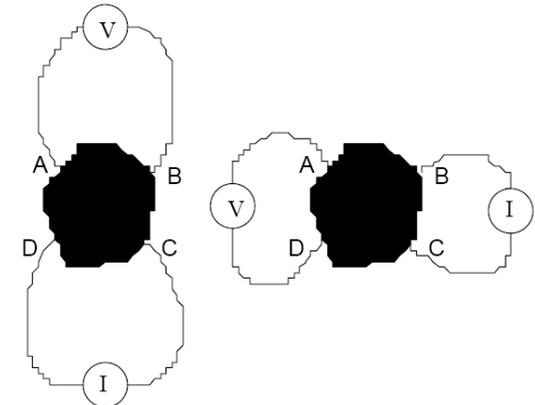
$$\rho = \frac{\pi}{\ln 2} W \frac{R_{ab-cd} + R_{bc-da}}{2} f$$



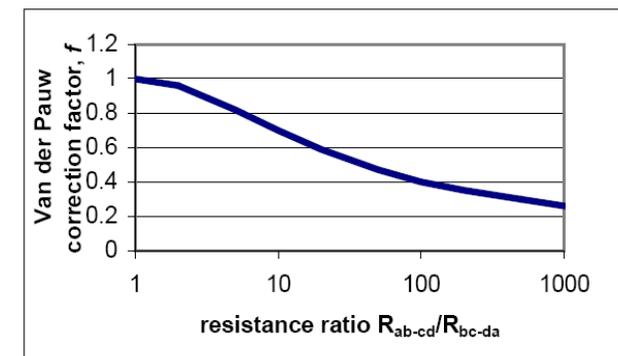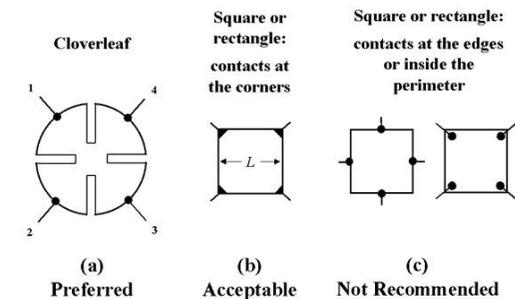The contact arrangements for the two resistance measurements, R_{ab-cd} and R_{bc-da} used in the Van der Pauw resistivity measurement.



Correction factor based on the ratio of the two resistance measurements, R_{ab-cd} and R_{bc-da} used in the Van der Pauw resistivity measurement.

Method for Measuring Electrical Resistivity of Anisotropic Materials

H. C. MONTGOMERY

Bell Telephone Laboratories, Incorporated, Murray Hill, New Jersey 07974

(Received 30 November 1970)


A rectangular prism with edges in principal crystal directions is prepared with electrodes on the corners of one face. Voltage-current ratios for opposite pairs of electrodes permit calculation of components of the resistivity tensor. The method can use small samples, and is best suited to materials describable by two or three tensor components. Examples are given of measurements of V_2O_5 -Cr and oriented amorphous graphite.



Montgomery technique

$$(\rho_2/\rho_1)^{1/2} = (l_2/l_1) \times (l_1'/l_2').$$

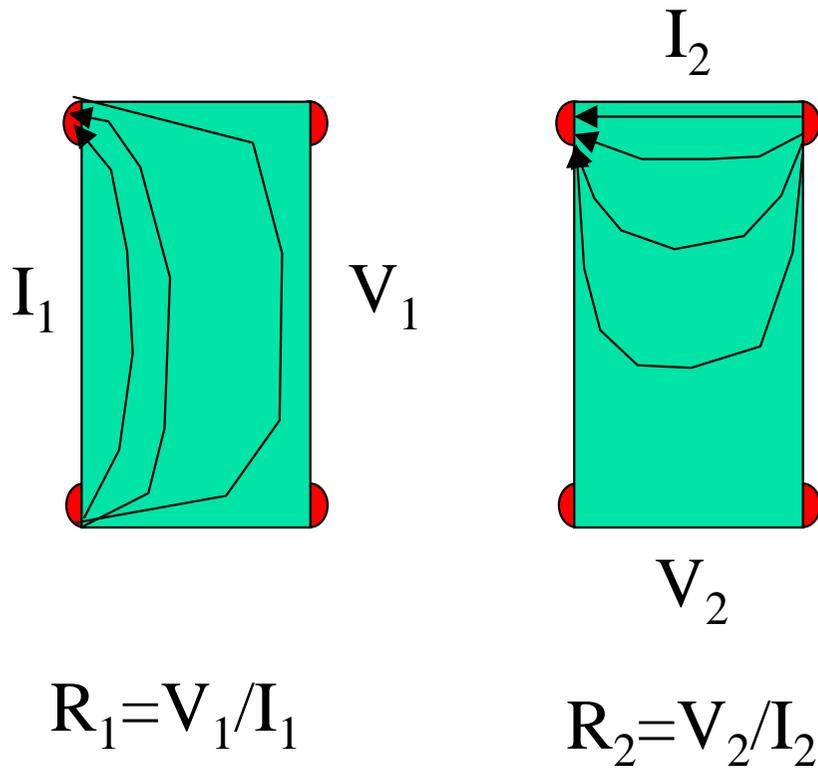1. Van der Pauw resistivity measurements on samples of rectangular



2. Calculation of the anisotropy ratio for isotropic samples

3. Scaling anisotropic samples on isotropic by van der Pauw scaling transformation

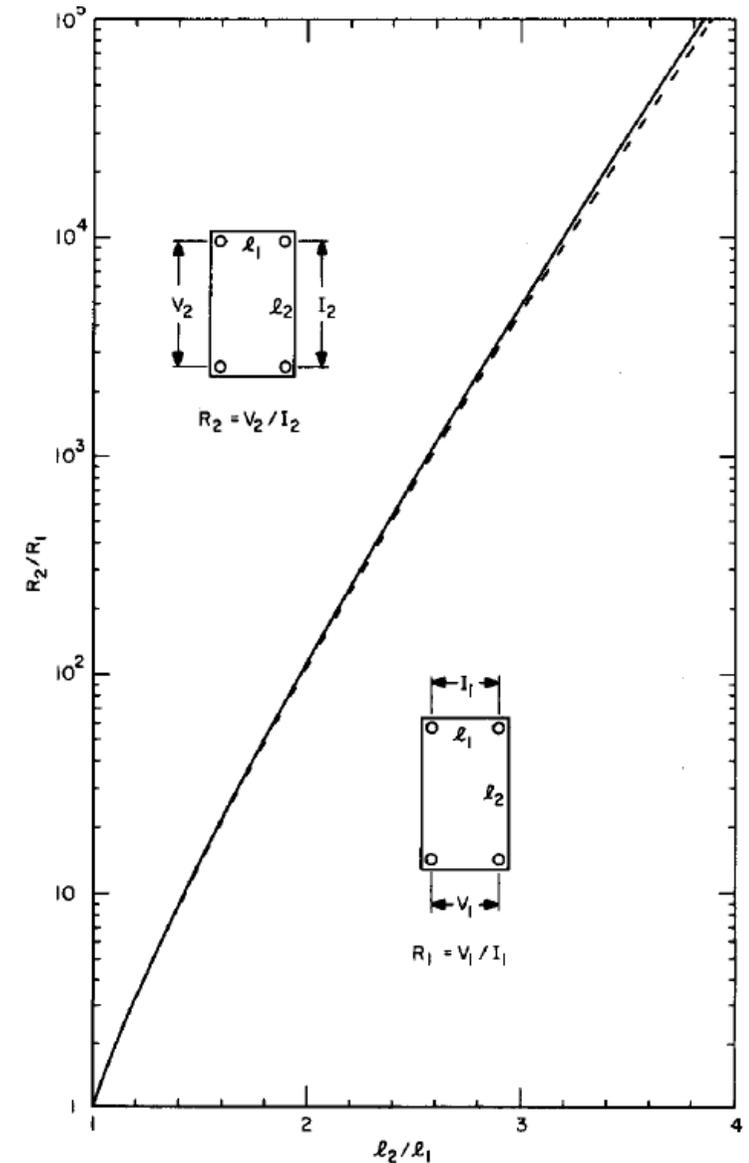


FIG. 3. Resistance ratio versus sample dimension ratio. Solid line is for a thin sample; dashed line for a thick sample. Details of thickness dependence given in Table II.



Interference Factor

- Ohmic contact quality and size
- Sample uniformity and accurate thickness determination
- Photoconductive and photovoltaic effects



Reading

1. Low Level Measurements Handbook, Keithley www.keithley.com
2. Lake Shore manual for LS370
3. J. M. Ziman, Principles of the Theory of Solids, 1964